

## ECE-111 Advanced Digital Design Projects

### Homework-3:

Develop SystemVerilog RTL model for 4-bit Johnson Counter and perform following mentioned :

- Synthesize Johnson counter
- Run simulation using Johnson counter testbench provided
- Review synthesis results (resource usage and RTL netlist/schematic)
  - Note : Explanation of resource usage in report is not mandatory to provide.
- Review input and output signals in simulation waveform.

### About Johnson Counter :

- Similar to Straight Ring counter with below mentioned difference
- Johnson counter connects the complement of the output of the last shift register to the input of the first register and circulates a stream of ones followed by zeros around the ring
- Johnson Counter has  $2N$  states (if  $N$  is 4, then total states for counting is 8. And 4-bit pattern will repeat after 8 cycles).

### 4-bit Johnson Counter with initial load count value = 4'b0000

| Johnson Counter |       |          |          |          |          |
|-----------------|-------|----------|----------|----------|----------|
| Clock Cycle     | State | count[3] | count[2] | count[1] | count[0] |
| 1               | 0     | 0        | 0        | 0        | 0        |
| 2               | 1     | 1        | 0        | 0        | 0        |
| 3               | 2     | 1        | 1        | 0        | 0        |
| 4               | 3     | 1        | 1        | 1        | 0        |
| 5               | 4     | 1        | 1        | 1        | 1        |
| 6               | 5     | 0        | 1        | 1        | 1        |
| 7               | 6     | 0        | 0        | 1        | 1        |
| 8               | 7     | 0        | 0        | 0        | 1        |
| 9               | 0     | 0        | 0        | 0        | 0        |

4-bit  
pattern  
repeats  
every 8  
cycles


### Homework Submission :

**Submit report (PDF file) which should include:**

- Snippet of SystemVerilog design code
- RTL netlist viewer schematic and Synthesis resource usage
  - Optional: Resource usage explanation and post mapping schematic
- Simulation snapshot and explain simulation result to confirm it works as a Johnson counter

### Note:

- When creating RTL model for Johnson Counter, name SystemVerilog Module name as : **johnson\_counter**
- **Assume below mentioned Primary Ports for Johnson Counter**
  - Input clk (clock)
  - Input clear (asynchronous reset / negedge signal)
  - Input preset (synchronous and active low singal)
  - Input load\_cnt (value gets loaded when !preset)
  - Output count (output count value)

 

Lab3.zip folder posted on Piazza and Canvas has **johnson\_counter\_testbench.sv** testbench code to simulate with johnson counter SystemVerilog module.

### Note :

- Assume initial load\_cnt signal value is set to 4'b0000 in testbench code provided.
- Students can update johnson\_counter\_testbench.sv code including initial load\_cnt value which can be changed or any other stimulus under initial block, and more.